

AQA A-Level Physics: Current Electricity – Calculation Questions

Praneel Physics

1. Calculate the current through a $12\ \Omega$ resistor with 36 V across it. (P)

Working and Answer:

$$I = \frac{V}{R} = \frac{36}{12} = 3\text{ A.}$$

2. Find the resistance when 0.5 A flows with 6 V applied. (P)

Working and Answer:

$$R = \frac{V}{I} = \frac{6}{0.5} = 12\ \Omega.$$

3. Calculate the power dissipated in a $8\ \Omega$ resistor with 4 A flowing. (P)

Working and Answer:

$$P = I^2 R = 4^2 \times 8 = 128\text{ W}.$$

4. Determine the charge flowing in 15 s with 2 A current. (P)

Working and Answer:

$$Q = It = 2 \times 15 = 30\text{ C}.$$

5. Calculate the energy transferred by 9 V moving 4 C of charge. (P)

Working and Answer:

$$E = VQ = 9 \times 4 = 36\text{ J}.$$

6. Find the potential difference across $5\ \Omega$ with $0.8\ A$ flowing. (P)

Working and Answer:

$$V = IR = 0.8 \times 5 = 4\ V.$$

7. A $3\ m$ wire of diameter $0.5\ mm$ has resistance $6\ \Omega$. Calculate its resistivity. (PP)

Working and Answer:

1. Area $A = \pi(0.25 \times 10^{-3})^2 = 1.96 \times 10^{-7}\ m^2$
2. $\rho = \frac{RA}{L} = \frac{6 \times 1.96 \times 10^{-7}}{3} = 3.93 \times 10^{-7}\ \Omega m.$

8. Calculate total resistance and current for $4\ \Omega$ and $6\ \Omega$ in series with 12 V . **(PP)**

Working and Answer:

1. $R_{total} = 4 + 6 = 10\ \Omega$
2. $I = \frac{12}{10} = 1.2\text{ A}$.

9. A 100 W bulb operates at 230 V . Find its resistance. **(PP)**

Working and Answer:

1. $P = \frac{V^2}{R}$
2. $R = \frac{230^2}{100} = 529\ \Omega$.

10. Calculate drift velocity for 2 A current in 1 mm² copper wire ($n = 8.5 \times 10^{28} \text{ m}^{-3}$). (PP)

Working and Answer:

$$\begin{aligned} 1. v &= \frac{I}{nAe} = \frac{2}{8.5 \times 10^{28} \times 10^{-6} \times 1.6 \times 10^{-19}} \\ 2. v &\approx 0.147 \text{ mm/s.} \end{aligned}$$

11. Find the emf when 3 A flows through 4 Ω with 0.5 Ω internal resistance. (PP)

Working and Answer:

$$1. \epsilon = I(R + r) = 3(4 + 0.5) = 13.5 \text{ V.}$$

12. Calculate energy stored in $470\ \mu F$ capacitor charged to $12\ V$. (PP)

Working and Answer:

1. $E = \frac{1}{2}CV^2 = 0.5 \times 470 \times 10^{-6} \times 144 = 0.0338\ J$.

13. A thermistor's resistance is $8\ k\Omega$ at $20^\circ C$ and $2\ k\Omega$ at $60^\circ C$. Find its resistance at $35^\circ C$ (linear assumption). (PPP)

Working and Answer:

1. Rate: $\frac{\Delta R}{\Delta T} = \frac{2000-8000}{60-20} = -150\ \Omega/^\circ C$
2. $R = 8000 + (-150)(35 - 20)$
3. $R = 8000 - 2250 = 5.75\ k\Omega$.

14. A potential divider uses $5\text{ k}\Omega$ and $10\text{ k}\Omega$ resistors with 15 V supply. Find V_{out} . (PPP)

Working and Answer:

1. Total resistance: $15\text{ k}\Omega$
2. Current: $I = \frac{15}{15000} = 1\text{ mA}$
3. $V_{out} = I \times 10000 = 10\text{ V}$.

15. A battery ($\epsilon = 6\text{ V}$, $r = 0.4\Omega$) powers a 5Ω resistor. Find the terminal pd. (PPP)

Working and Answer:

1. Current: $I = \frac{6}{5+0.4} \approx 1.11\text{ A}$
2. Terminal pd: $V = 6 - (1.11 \times 0.4) \approx 5.56\text{ V}$.

16. Calculate resistivity of a 4 m wire with 0.8 mm^2 area and 3.2Ω resistance. (PPP)

Working and Answer:

$$\begin{aligned} 1. \rho &= \frac{RA}{L} = \frac{3.2 \times 0.8 \times 10^{-6}}{4} \\ 2. \rho &= 6.4 \times 10^{-7} \Omega\text{m}. \end{aligned}$$

17. A 60 W bulb operates at 240 V . Find its resistance and current. (PPP)

Working and Answer:

$$\begin{aligned} 1. R &= \frac{V^2}{P} = \frac{240^2}{60} = 960\Omega \\ 2. I &= \frac{P}{V} = \frac{60}{240} = 0.25\text{ A}. \end{aligned}$$

18. A capacitor charges to 9 V with 45 mC . Calculate its capacitance. (PPP)

Working and Answer:

1. $C = \frac{Q}{V} = \frac{45 \times 10^{-3}}{9} = 5\text{ mF}.$

19. A battery ($\epsilon = 12\text{ V}$, $r = 0.8\ \Omega$) supplies parallel $3\ \Omega$ and $6\ \Omega$ resistors. Calculate total power dissipated. (PPPP)

Working and Answer:

1. Parallel resistance: $R_p = (1/3 + 1/6)^{-1} = 2\ \Omega$
2. Total resistance: $2 + 0.8 = 2.8\ \Omega$
3. Current: $I = \frac{12}{2.8} \approx 4.29\text{ A}$
4. Power: $P = I^2 R_p \approx 4.29^2 \times 2 \approx 36.8\text{ W}.$

20. A copper wire ($\rho = 1.7 \times 10^{-8} \Omega m$, diameter 1 mm) carries 3 A . Calculate electric field strength. (PPPP)

Working and Answer:

1. Area: $A = \pi(0.5 \times 10^{-3})^2 = 7.85 \times 10^{-7} \text{ m}^2$
2. Resistance per meter: $\frac{R}{L} = \frac{\rho}{A} \approx 0.0217 \Omega/m$
3. Potential gradient: $\frac{V}{L} = I \frac{R}{L} = 3 \times 0.0217 \approx 0.065 \text{ V/m}$
4. Electric field: $E = 0.065 \text{ V/m}$.

21. A capacitor ($100\mu F$) discharges through $10k\Omega$. Calculate time for charge to halve.
(PPPP)

Working and Answer:

1. Time constant: $\tau = RC = 10000 \times 100 \times 10^{-6} = 1\text{ s}$
2. $t_{1/2} = \tau \ln 2 \approx 0.693\text{ s}$.

22. A Wheatstone bridge has $R_1 = 120\Omega$, $R_2 = 240\Omega$, $R_3 = 180\Omega$. Find R_4 for balance.
(PPPP)

Working and Answer:

1. Balance condition: $\frac{R_1}{R_2} = \frac{R_3}{R_4}$
2. $R_4 = R_3 \times \frac{R_2}{R_1} = 180 \times 2 = 360\Omega$.

23. A 24 V battery powers series $6\,\Omega$ and parallel $4\,\Omega + 12\,\Omega$ resistors. Find the current. (PPPP)

Working and Answer:

1. Parallel resistance: $R_p = (1/4 + 1/12)^{-1} = 3\,\Omega$
2. Total resistance: $6 + 3 = 9\,\Omega$
3. Current: $I = \frac{24}{9} \approx 2.67\text{ A}$.

24. A 0.2 mm diameter gold wire ($\rho = 2.4 \times 10^{-8} \Omega\text{m}$) carries 0.8 A . Find power dissipated per meter. (PPPP)

Working and Answer:

1. Area: $A = \pi(0.1 \times 10^{-3})^2 = 3.14 \times 10^{-8} \text{ m}^2$
2. Resistance per meter: $\frac{R}{L} = \frac{\rho}{A} \approx 0.764 \Omega/\text{m}$
3. Power: $P = I^2 R \approx 0.8^2 \times 0.764 \approx 0.489 \text{ W/m}$.

25. A capacitor ($470\ \mu F$) discharges through $2.2\ k\Omega$. Calculate time for energy to reach 25% of initial. (PPPPP)

Working and Answer:

1. Energy $\propto V^2$, so need $V = 0.5V_0$
2. Discharge equation: $0.5 = e^{-t/RC}$
3. $t = -RC \ln 0.5 \approx 0.693 \times 2200 \times 470 \times 10^{-6}$
4. $t \approx 0.717\ s$.

26. A non-ohmic device follows $I = 0.01V^2$. Calculate dynamic resistance at 10 V. (PPPPP)

Working and Answer:

1. Differentiate: $\frac{dI}{dV} = 0.02V$
2. At 10 V: $\frac{dI}{dV} = 0.2 \text{ A/V}$
3. Dynamic resistance: $R = 1/(dI/dV) = 5 \Omega$.

27. A battery ($\epsilon = 15\text{ V}$, $r = 0.6\ \Omega$) supplies parallel $3\ \Omega$ and $6\ \Omega$ in series with $2\ \Omega$. Find terminal pd. (PPPPP)

Working and Answer:

1. Parallel resistance: $R_p = (1/3 + 1/6)^{-1} = 2\ \Omega$
2. Total resistance: $2 + 2 + 0.6 = 4.6\ \Omega$
3. Current: $I = \frac{15}{4.6} \approx 3.26\text{ A}$
4. Terminal pd: $V = 15 - (3.26 \times 0.6) \approx 13.04\text{ V}$.

28. A thermistor ($R_{25^\circ C} = 10\text{ k}\Omega$, $R_{75^\circ C} = 2\text{ k}\Omega$) is used in a potential divider with $8\text{ k}\Omega$ resistor and 12 V supply. Find V_{out} at $50^\circ C$ (linear). (PPPPP)

Working and Answer:

1. Rate: $\frac{\Delta R}{\Delta T} = \frac{2000-10000}{75-25} = -160\text{ }\Omega/^\circ C$
2. $R_{50^\circ C} = 10000 + (-160)(50 - 25) = 6\text{ k}\Omega$
3. $V_{out} = 12 \times \frac{8000}{8000+6000} \approx 6.86\text{ V}$.

29. A 0.05 mm^2 carbon wire ($\rho = 6 \times 10^{-5} \Omega \text{ m}$) carries 20 mA . Calculate power density (W/m^3). (PPPPP)

Working and Answer:

1. Resistance per meter: $\frac{R}{L} = \frac{\rho}{A} = \frac{6 \times 10^{-5}}{5 \times 10^{-8}} = 1200 \Omega/\text{m}$
2. Power per meter: $P = I^2 R = (0.02)^2 \times 1200 = 0.48 \text{ W/m}$
3. Volume per meter: $V = 5 \times 10^{-8} \text{ m}^3$
4. Power density: $\frac{0.48}{5 \times 10^{-8}} = 9.6 \times 10^6 \text{ W/m}^3$.

30. A capacitor (C) discharges from 12 V to 3 V in 4 s through $1\text{ M}\Omega$. Find C . (PPPPP)

Working and Answer:

1. Discharge equation: $3 = 12e^{-4/RC}$
2. $0.25 = e^{-4/RC}$
3. $\ln 0.25 = -4/RC$
4. $RC = \frac{4}{\ln 4} \approx 2.89\text{ s}$
5. $C = \frac{2.89}{10^6} \approx 2.89\text{ }\mu\text{F}$.