

# Edexcel AS Physics: Electric Circuits – Calculation Practice

Praneel Physics

1. A circuit has a current of 2 A flowing through a resistor of  $5\ \Omega$ . What is the voltage across the resistor? (P)

*Working and Answer:*

Using Ohm's Law,  $V = I \times R$ . Thus,  $V = 2\text{ A} \times 5\ \Omega = 10\text{ V}$ .

2. A battery provides a voltage of 12 V and is connected to a resistor of  $4\Omega$ . Calculate the current flowing through the circuit. (P)

*Working and Answer:*

Using Ohm's Law,  $I = \frac{V}{R}$ . Thus,  $I = \frac{12\text{ V}}{4\Omega} = 3\text{ A}$ .

3. If a circuit has a total resistance of  $10\Omega$  and a current of 0.5 A, what is the voltage supplied by the battery? (P)

*Working and Answer:*

Using Ohm's Law,  $V = I \times R$ . Thus,  $V = 0.5\text{ A} \times 10\Omega = 5\text{ V}$ .

4. A resistor of  $20\ \Omega$  has a current of  $0.25\text{ A}$  flowing through it. What is the power dissipated by the resistor? (P)

*Working and Answer:*

Using the power formula,  $P = I^2 \times R$ . Thus,  $P = (0.25\text{ A})^2 \times 20\ \Omega = 1.25\text{ W}$ .

5. A circuit has a voltage of  $9\text{ V}$  and a current of  $3\text{ A}$ . What is the resistance in the circuit? (P)

*Working and Answer:*

Using Ohm's Law,  $R = \frac{V}{I}$ . Thus,  $R = \frac{9\text{ V}}{3\text{ A}} = 3\ \Omega$ .

6. A circuit contains two resistors in series:  $4\Omega$  and  $6\Omega$ . What is the total resistance? (PP)

*Working and Answer:*

For resistors in series,  $R_{\text{total}} = R_1 + R_2$ . Thus,  $R_{\text{total}} = 4\Omega + 6\Omega = 10\Omega$ .

7. In a parallel circuit, two resistors of  $8\Omega$  and  $12\Omega$  are connected. What is the total resistance? (PP)

*Working and Answer:*

Using the formula for parallel resistors,  $\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2}$ . Thus,  
$$\frac{1}{R_{\text{total}}} = \frac{1}{8} + \frac{1}{12} = \frac{3}{24} + \frac{2}{24} = \frac{5}{24}$$
. Therefore,  $R_{\text{total}} = \frac{24}{5} = 4.8\Omega$ .

8. A  $10\ \Omega$  resistor is connected in series with a  $15\ \Omega$  resistor. If the total current is 2 A, what is the voltage across the  $15\ \Omega$  resistor? (PP)

*Working and Answer:*

Total resistance  $R_{\text{total}} = 10\ \Omega + 15\ \Omega = 25\ \Omega$ . Voltage across  $15\ \Omega$  is  $V = I \times R = 2\ \text{A} \times 15\ \Omega = 30\ \text{V}$ .

9. A circuit has a total voltage of 24 V and contains three resistors in series:  $5\ \Omega$ ,  $10\ \Omega$ , and  $15\ \Omega$ . What is the current flowing through the circuit? (PP)

*Working and Answer:*

Total resistance  $R_{\text{total}} = 5\ \Omega + 10\ \Omega + 15\ \Omega = 30\ \Omega$ . Current  $I = \frac{V}{R} = \frac{24\ \text{V}}{30\ \Omega} = 0.8\ \text{A}$ .

10. In a parallel circuit with a  $6\Omega$  and a  $3\Omega$  resistor, if the voltage across the circuit is 12 V, what is the total current flowing through the circuit? (PP)

*Working and Answer:*

Using  $I = \frac{V}{R}$  for each resistor:  $I_1 = \frac{12\text{ V}}{6\Omega} = 2\text{ A}$  and  $I_2 = \frac{12\text{ V}}{3\Omega} = 4\text{ A}$ . Total current  $I_{\text{total}} = I_1 + I_2 = 2\text{ A} + 4\text{ A} = 6\text{ A}$ .

11. A  $100\Omega$  resistor is connected in series with a  $200\Omega$  resistor. If the total current is 0.1 A, what is the power dissipated by the  $200\Omega$  resistor? (PPP)

*Working and Answer:*

Total resistance  $R_{\text{total}} = 100\Omega + 200\Omega = 300\Omega$ . Voltage across  $200\Omega$  is  $V = I \times R = 0.1\text{ A} \times 200\Omega = 20\text{ V}$ . Power  $P = \frac{V^2}{R} = \frac{20^2}{200} = 2\text{ W}$ .

12. A circuit has a total voltage of 48 V and contains two resistors in series:  $20\ \Omega$  and  $30\ \Omega$ . What is the voltage across the  $30\ \Omega$  resistor? (PPP)

*Working and Answer:*

Total resistance  $R_{\text{total}} = 20\ \Omega + 30\ \Omega = 50\ \Omega$ . Current  $I = \frac{48\ \text{V}}{50\ \Omega} = 0.96\ \text{A}$ . Voltage across  $30\ \Omega$  is  $V = I \times R = 0.96\ \text{A} \times 30\ \Omega = 28.8\ \text{V}$ .

13. In a parallel circuit with a  $4\ \Omega$  and a  $6\ \Omega$  resistor, if the total current is 5 A, what is the voltage across the circuit? (PPP)

*Working and Answer:*

Using  $I = \frac{V}{R}$  for each resistor:  $I_1 = \frac{V}{4}$  and  $I_2 = \frac{V}{6}$ . Total current  $I_{\text{total}} = I_1 + I_2 = \frac{V}{4} + \frac{V}{6}$ . Solving gives  $V = 12\ \text{V}$ .

14. A  $50\Omega$  resistor is connected in series with a  $100\Omega$  resistor. If the total voltage is 60 V, what is the power dissipated by the  $50\Omega$  resistor? (PPP)

*Working and Answer:*

$$\text{Total resistance } R_{\text{total}} = 50\Omega + 100\Omega = 150\Omega. \text{ Current } I = \frac{60\text{ V}}{150\Omega} = 0.4\text{ A.}$$
$$\text{Power } P = I^2 \times R = (0.4\text{ A})^2 \times 50\Omega = 8\text{ W.}$$

15. A circuit has three resistors in series:  $10\Omega$ ,  $20\Omega$ , and  $30\Omega$ . If the total current is 2 A, what is the total power dissipated in the circuit? (PPPP)

*Working and Answer:*

$$\text{Total resistance } R_{\text{total}} = 10\Omega + 20\Omega + 30\Omega = 60\Omega. \text{ Voltage } V = I \times R_{\text{total}} = 2\text{ A} \times 60\Omega = 120\text{ V. Power}$$
$$P = I^2 \times R_{\text{total}} = (2\text{ A})^2 \times 60\Omega = 240\text{ W.}$$

16. In a parallel circuit with a  $12\Omega$  and a  $4\Omega$  resistor, if the voltage across the circuit is 24 V, what is the total current flowing through the circuit? (PPPP)

*Working and Answer:*

Using  $I = \frac{V}{R}$  for each resistor:  $I_1 = \frac{24\text{ V}}{12\Omega} = 2\text{ A}$  and  $I_2 = \frac{24\text{ V}}{4\Omega} = 6\text{ A}$ . Total current  $I_{\text{total}} = I_1 + I_2 = 2\text{ A} + 6\text{ A} = 8\text{ A}$ .

17. A  $100\Omega$  resistor is connected in series with a  $200\Omega$  resistor. If the total voltage is 120 V, what is the voltage across the  $200\Omega$  resistor? (PPPP)

*Working and Answer:*

Total resistance  $R_{\text{total}} = 100\Omega + 200\Omega = 300\Omega$ . Current  $I = \frac{120\text{ V}}{300\Omega} = 0.4\text{ A}$ . Voltage across  $200\Omega$  is  $V = I \times R = 0.4\text{ A} \times 200\Omega = 80\text{ V}$ .

18. A circuit has a total voltage of 36 V and contains three resistors in series:  $10\ \Omega$ ,  $20\ \Omega$ , and  $30\ \Omega$ . What is the current flowing through the circuit? (PPPP)

*Working and Answer:*

$$\text{Total resistance } R_{\text{total}} = 10\ \Omega + 20\ \Omega + 30\ \Omega = 60\ \Omega. \text{ Current } I = \frac{36\ \text{V}}{60\ \Omega} = 0.6\ \text{A.}$$

19. In a parallel circuit with a  $5\ \Omega$  and a  $15\ \Omega$  resistor, if the total current is 3 A, what is the voltage across the circuit? (PPPP)

*Working and Answer:*

$$\text{Using } I = \frac{V}{R} \text{ for each resistor: } I_1 = \frac{V}{5} \text{ and } I_2 = \frac{V}{15}. \text{ Total current } I_{\text{total}} = I_1 + I_2 = \frac{V}{5} + \frac{V}{15}. \text{ Solving gives } V = 15\ \text{V.}$$

20. A  $50\Omega$  resistor is connected in series with a  $100\Omega$  resistor. If the total voltage is 150 V, what is the power dissipated by the  $100\Omega$  resistor? (PPPPP)

*Working and Answer:*

$$\text{Total resistance } R_{\text{total}} = 50\Omega + 100\Omega = 150\Omega. \text{ Current } I = \frac{150\text{ V}}{150\Omega} = 1\text{ A.}$$
$$\text{Power } P = I^2 \times R = (1\text{ A})^2 \times 100\Omega = 100\text{ W.}$$

21. A circuit has three resistors in series:  $10\Omega$ ,  $20\Omega$ , and  $30\Omega$ . If the total current is 1.5 A, what is the total power dissipated in the circuit? (PPPPP)

*Working and Answer:*

$$\text{Total resistance } R_{\text{total}} = 10\Omega + 20\Omega + 30\Omega = 60\Omega. \text{ Voltage}$$
$$V = I \times R_{\text{total}} = 1.5\text{ A} \times 60\Omega = 90\text{ V. Power}$$
$$P = I^2 \times R_{\text{total}} = (1.5\text{ A})^2 \times 60\Omega = 135\text{ W.}$$

22. In a parallel circuit with a  $12\Omega$  and a  $6\Omega$  resistor, if the voltage across the circuit is 24 V, what is the total current flowing through the circuit? (PPPPP)

*Working and Answer:*

Using  $I = \frac{V}{R}$  for each resistor:  $I_1 = \frac{24\text{ V}}{12\Omega} = 2\text{ A}$  and  $I_2 = \frac{24\text{ V}}{6\Omega} = 4\text{ A}$ . Total current  $I_{\text{total}} = I_1 + I_2 = 2\text{ A} + 4\text{ A} = 6\text{ A}$ .

23. A  $100\Omega$  resistor is connected in series with a  $200\Omega$  resistor. If the total voltage is 240 V, what is the voltage across the  $100\Omega$  resistor? (PPPPP)

*Working and Answer:*

Total resistance  $R_{\text{total}} = 100\Omega + 200\Omega = 300\Omega$ . Current  $I = \frac{240\text{ V}}{300\Omega} = 0.8\text{ A}$ . Voltage across  $100\Omega$  is  $V = I \times R = 0.8\text{ A} \times 100\Omega = 80\text{ V}$ .

24. A circuit has a total voltage of 48 V and contains three resistors in series:  $10\ \Omega$ ,  $20\ \Omega$ , and  $30\ \Omega$ . What is the current flowing through the circuit? (PPPPP)

*Working and Answer:*

$$\text{Total resistance } R_{\text{total}} = 10\ \Omega + 20\ \Omega + 30\ \Omega = 60\ \Omega. \text{ Current } I = \frac{48\ \text{V}}{60\ \Omega} = 0.8\ \text{A.}$$